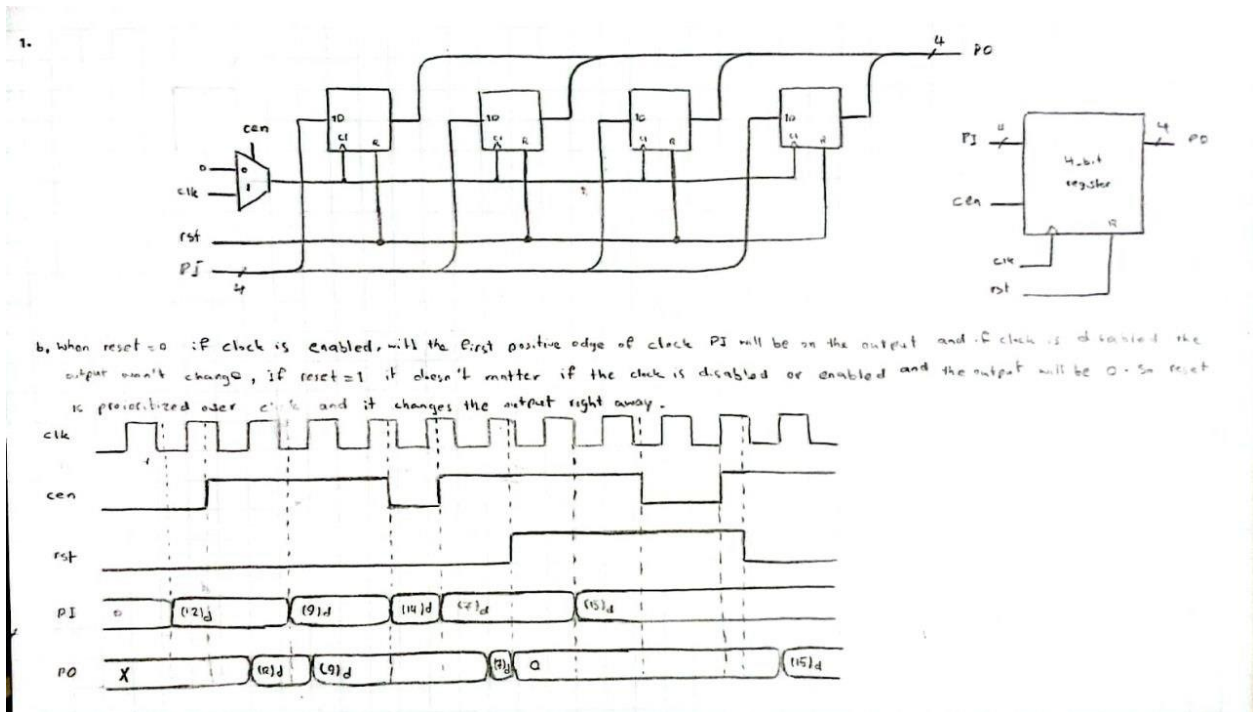


1.



```

1  `timescale 1ns/1ns
2
3  module register4(input [3:0] PI , input clk , cen , rst , output reg [3:0] PO);
4      always @ (posedge clk , posedge rst) begin
5          if (rst) PO <= 4'd0;
6          else if (cen) PO <= PI;
7      end
8  endmodule
9

```



```


1 | `timescale 1ns/1ns
2 |
3 | module shifter (input [3:0] si , input clk , shn , rst , output reg [3:0] so);
4 |     wire [3:0] stage [0:7];
5 |
6 |     genvar i;
7 |     generate
8 |         for (i = 0; i < 8; i = i + 1) begin : shift_stage
9 |             if (i == 0) begin
10 |                 register4 stage_reg (si , clk , shn , rst , stage[i]);
11 |             end else begin
12 |                 register4 stage_reg (stage[i-1] , clk , shn , rst , stage[i]);
13 |             end
14 |         end
15 |     endgenerate
16 |
17 |     assign so = stage[7];
18 |
19 | endmodule
20 |

```

```

1 | `timescale 1ns/1ns
2 |
3 | module shifter_tb();
4 |     reg [3:0] si;
5 |     reg clk = 1'b0;
6 |     reg shn;
7 |     reg rst;
8 |
9 |     wire [3:0] so;
10 |
11 |     shifter UUT(si , clk , shn , rst , so);
12 |
13 |     always #5 clk <= ~clk;
14 |
15 |     initial begin
16 |         si = 4'b0000;
17 |         shn = 1'b0;
18 |         rst = 1'b1;
19 |         #10 rst = 1'b0;
20 |         si = 4'b1010;
21 |         shn = 1'b1;
22 |
23 |         #80 shn = 1'b0;
24 |         si = 4'b0000;
25 |
26 |         #20 si = 4'b1100;
27 |         shn = 1'b1;
28 |
29 |         #80 si = 4'b0110;
30 |         shn = 1'b0;
31 |
32 |         #80 $stop;
33 |     end
34 | endmodule
35 |

```

 

3.

a.

```


1  `timescale 1ns/1ns
2
3  module shifter_nonb(input [3:0] si , input clk , shn , rst , output reg [3:0] so);
4      reg [3:0] s_array [0:7];
5      integer i;
6
7      always @(posedge clk or posedge rst) begin
8          if (rst) begin
9              for (i = 0; i < 8; i = i + 1) begin
10                 s_array[i] <= 4'd0;
11             end
12         end
13         else if (shn) begin
14             s_array[0] <= si;
15             for (i = 7; i > 0; i = i - 1) begin
16                 s_array[i] <= s_array[i-1];
17             end
18         end
19     end
20
21     assign so = s_array[7];
22
23 endmodule
24
25

```

```

1 | `timescale 1ns/1ns
2 |
3 | module shifter_nonb_tb();
4 |     reg [3:0] si;
5 |     reg clk = 1'b0;
6 |     reg shn;
7 |     reg rst;
8 |     wire [3:0] so;
9 |
10 |     shifter_nonb UUT(si, clk, shn, rst, so);
11 |
12 |     always #5 clk = ~clk;
13 |
14 |     initial begin
15 |         si = 4'b0000;
16 |         shn = 0;
17 |         rst = 1;
18 |         #10 rst = 0;
19 |         #10 shn = 1;
20 |         si = 4'b1010;
21 |         #80 shn = 0;
22 |         #20 si = 4'b1100;
23 |         shn = 1;
24 |         #80 shn = 0;
25 |         #20 $stop;
26 |     end
27 | endmodule
28 |
29 |

```

 

b.

```


1  `timescale 1ns/1ns
2
3  module shifter_b(input [3:0] si , input clk , shn , rst , output reg [3:0] so);
4      reg [3:0] s_array [0:7];
5      integer i;
6
7      always @(posedge clk or posedge rst) begin
8          if (rst) begin
9              for (i = 0; i < 8; i = i + 1) begin
10                 s_array[i] = 4'd0;
11             end
12         end
13         else if (shn) begin
14             s_array[0] = si;
15             for (i = 7; i > 0; i = i - 1) begin
16                 s_array[i] = s_array[i-1];
17             end
18         end
19     end
20
21     assign so = s_array[7];
22
23 endmodule
24

```

```

1  `timescale 1ns/1ns
2
3  module shifter_b_tb();
4      reg [3:0] si;
5      reg clk = 1'b0;
6      reg shn;
7      reg rst;
8      wire [3:0] so;
9
10     shifter_b uut(si , clk , rst , shn , so);
11
12     always #5 clk = ~clk;
13
14     initial begin
15         si = 4'b0000;
16         shn = 1'b0;
17         rst = 1'b1;
18         #10 rst = 1'b0;
19         #10 si = 4'b1010;
20         shn = 1'b1;
21         #80 shn = 1'b0;
22         si = 4'b0000;
23         #20 si = 4'b1100;
24         shn = 1'b1;
25         #80 shn = 1'b0;
26         #20 $stop;
27     end
28 endmodule
29

```

 

C.

3. c. When we use blocking method (`=`) the target variable will be updated right away during the simulation but in non-blocking assignment (`=>`) variables will be updated at the end of each cycle in simulation and it's better for describing sequential logic.